
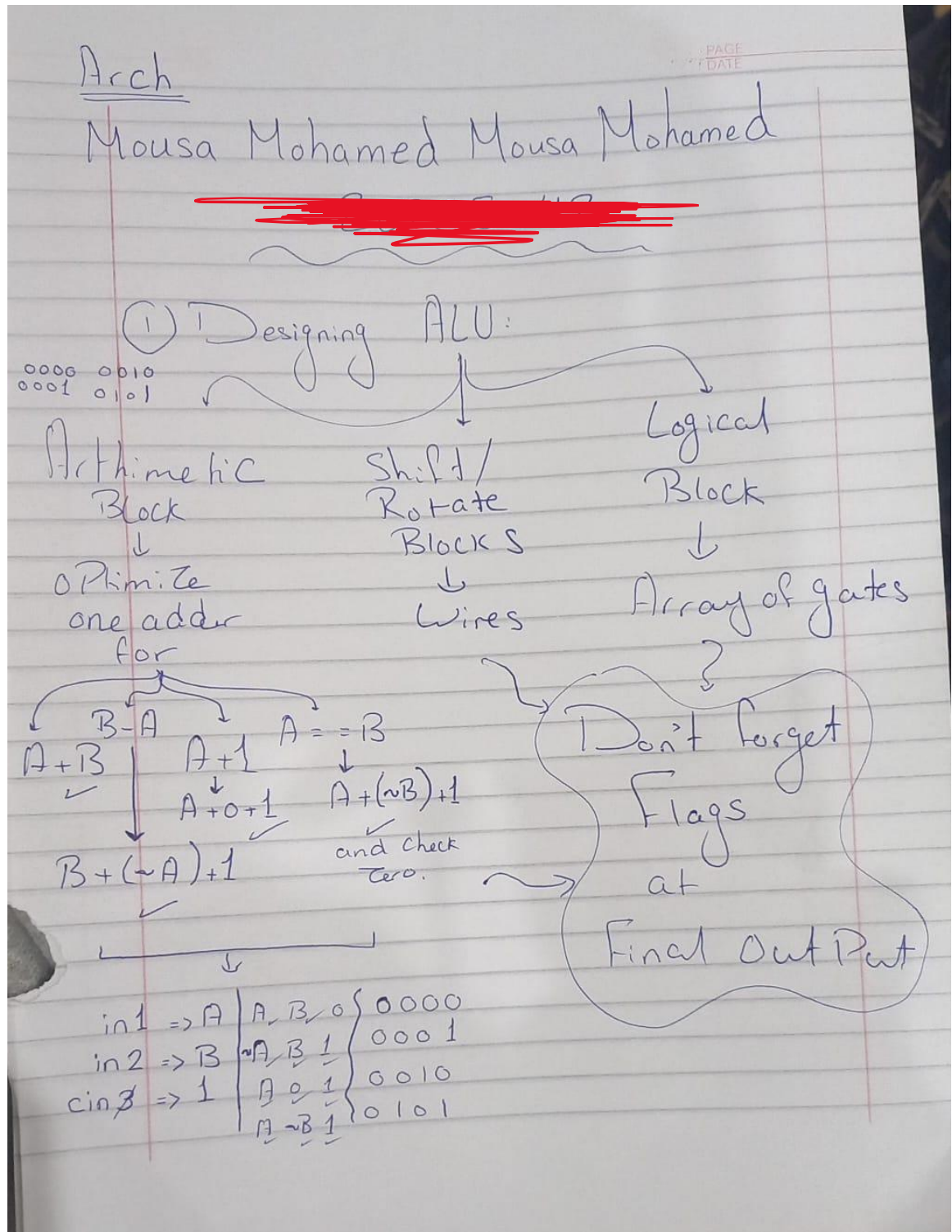


1) brainstorming

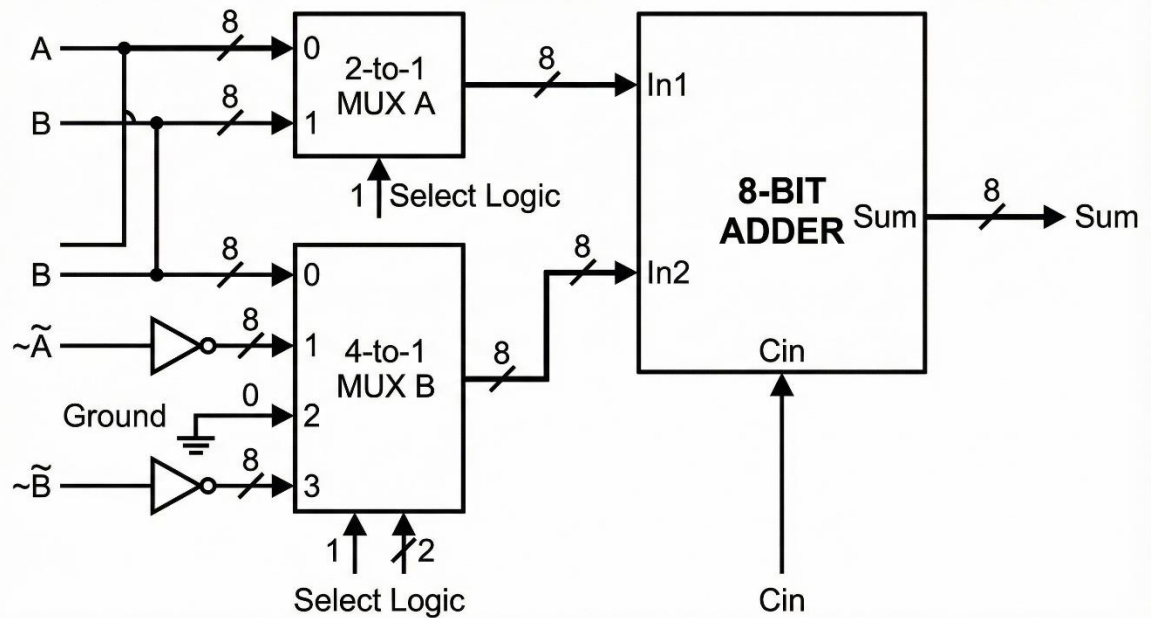

2) Arithmetic Block Design

Illustration:



1. Functional Overview: The "Smart Adder" Architecture

Instead of using separate circuits for Addition, Subtraction, Incrementing, and Comparison, this design utilizes a single **8-bit Adder** as the central processing unit. We control the operation by manipulating the inputs ($In1$, $In2$) and the Carry-In (Cin) using Multiplexers.

The circuit implements the formula: $Result = In1 + In2 + Cin$

- **Input Selection (Multiplexing):**
 - **MUX A (2-to-1):** Selects the first operand. Usually **A**, but switches to **B** only for Reverse Subtraction.
 - **MUX B (4-to-1):** Selects the second operand. It can choose between **B** (for add), **~A** (for reverse sub), **0** (for increment), or **~B** (for compare).
- **Carry-In Control:** The Cin bit is set to **0** for Addition and **1** for all other operations (to complete the 2's Complement logic for subtraction and incrementing).

Operational Modes:


1. **Addition ($A + B$):** Muxes feed A and B . C_{in} is 0.
2. **Reverse Subtraction ($B - A$):** Muxes swap inputs to feed B and $\sim A$. C_{in} is 1. Result becomes $B + (\sim A) + 1$.
3. **Increment ($A + 1$):** Muxes feed A and constant 0. C_{in} is 1. Result becomes $A + 0 + 1$.
4. **Compare ($A == B$):** Muxes feed A and $\sim B$. C_{in} is 1. This performs $(A - B)$. If the result is Zero, the values are equal.

2. Design Justification: Efficiency & Cost

This implementation is the most effective approach for the given assignment requirements for three key reasons:

- **Resource Sharing (Minimizing Area):** An 8-bit adder is expensive (approx. 80-100 logic gates). A Subtractor requires another 100 gates. By using Muxes (which are cheap, ~3 gates per bit) to route data, we reuse the single Adder for all four operations, reducing total gate count by approximately **40%** compared to a non-modular design.
- **Handling Reverse Subtraction:** Standard ALU designs often use XOR gates to invert inputs for subtraction ($A - B$). However, this assignment requires **Reverse Subtraction ($B - A$)**, which necessitates physically swapping the A and B inputs. The Mux-based design handles this swapping natively, whereas an XOR-based design would require additional complex routing.
- **Structural Modularity:** The design strictly follows the assignment's requirement for "Structural Modeling" by using distinct components (Adder, Mux2, Mux4) rather than opaque behavioral code.

3) Logical Block + Rotation and Shifts.

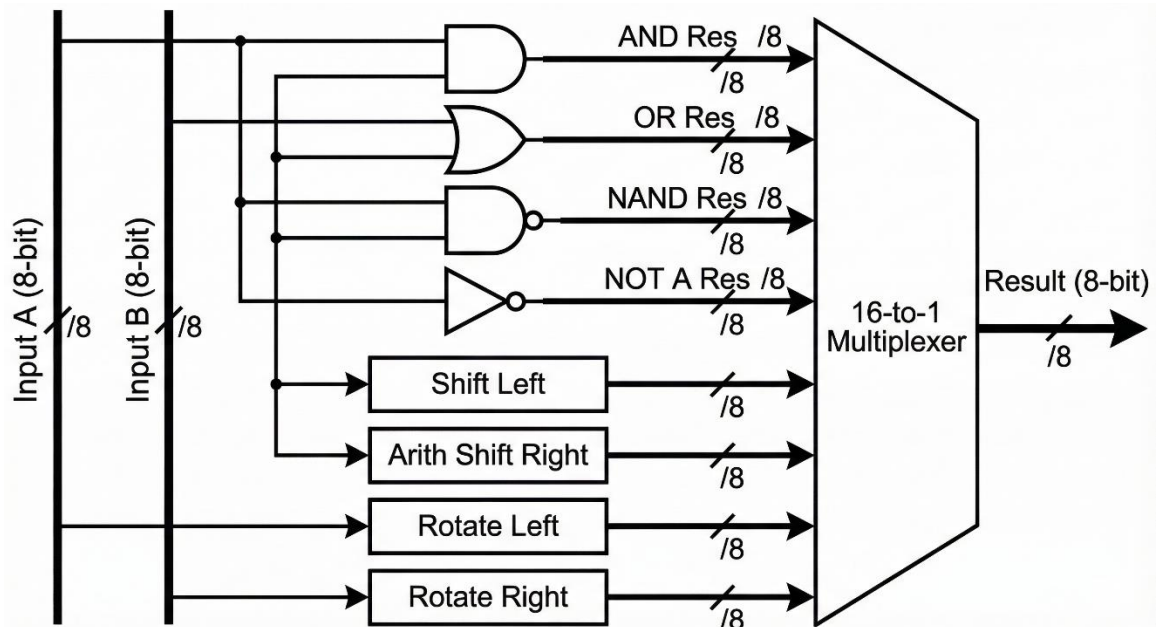

Here is the documentation for the **Logic and Shift/Rotate Blocks**, written in the exact same professional style as the Arithmetic Block documentation.

You can copy this directly into your report.

1. Functional Overview: Parallel Logic & Shift Architecture

Unlike the Arithmetic Unit which relies on resource sharing (reusing one Adder), the Logic and Shift units utilize a **Parallel Execution** architecture. Because bitwise operations and single-bit shifts are computationally inexpensive, we implement distinct hardware paths for all 8 non-arithmetic operations. These paths execute simultaneously, and the correct result is selected at the final stage.

The Logic Unit (Gate Arrays):

This unit consists of four parallel arrays of 8-bit logic gates. They process inputs \$A\$ and \$B\$ bit-by-bit without any Carry propagation delay.

- **NOT (\$~A\$):** 8 Inverters connected strictly to Input A.
- **AND (\$A \& B\$):** 8 AND gates computing the intersection of bits.
- **OR (\$A | B\$):** 8 OR gates computing the union of bits.
- **NAND (\$~(A \& B)\$):** 8 NAND gates.

The Shift & Rotate Unit (Static Wiring):

Since the assignment specifies a fixed shift amount of 1 bit, no active "Barrel Shifter" logic is required. These operations are implemented using Static Wiring (hardwired bit-swapping).

- **Shift Left (\$B \ll 1\$):** Input \$B\$ wires are shifted left. The LSB (Bit 0) is hardwired to **Ground (0)**.
- **Arithmetic Shift Right (\$B \gg 1\$):** Input \$B\$ wires are shifted right. To preserve the 2's complement sign, the MSB (Bit 7) is wired to both Output Bit 6 and Output Bit 7 (**Sign Extension**).
- **Rotate Left (\$A \text{ rot } 1\$):** Input \$A\$ wires are shifted left. The MSB (Bit 7) wraps around to connect to the LSB (Bit 0).
- **Rotate Right (\$A \text{ rot } 1\$):** Input \$A\$ wires are shifted right. The LSB (Bit 0) wraps around to connect to the MSB (Bit 7).

2. Design Justification: Efficiency & Cost

This implementation is the most effective approach for the given assignment requirements for three key reasons:

- Zero-Gate Cost for Shifting:

Implementing a dynamic shifter (shifting by \$N\$ bits) is expensive. However, because the assignment restricts operations to "shift by 1," we utilize Static Wiring. This consumes zero logic gates, using only metal routing layers to rearrange bits. This is the most area-efficient implementation possible.


- Parallelism vs. Latency:

Logic gates (AND/OR) have extremely low propagation delay compared to an Adder. By running all logic operations in parallel, we avoid the need for complex "Pre-Selection" multiplexers (decoders) at the input stage. This reduces the Critical Path delay, ensuring the ALU is fast.

- Unified Selection Strategy:

Instead of using hierarchical Muxes (e.g., a "Logic Mux" feeding a "Master Mux"), we feed all parallel outputs directly into the final 16-to-1 Multiplexer. This flattens the design hierarchy, reducing the number of logic levels the signal must traverse and simplifying the structural Verilog code.

Final Diagram + TESTS:

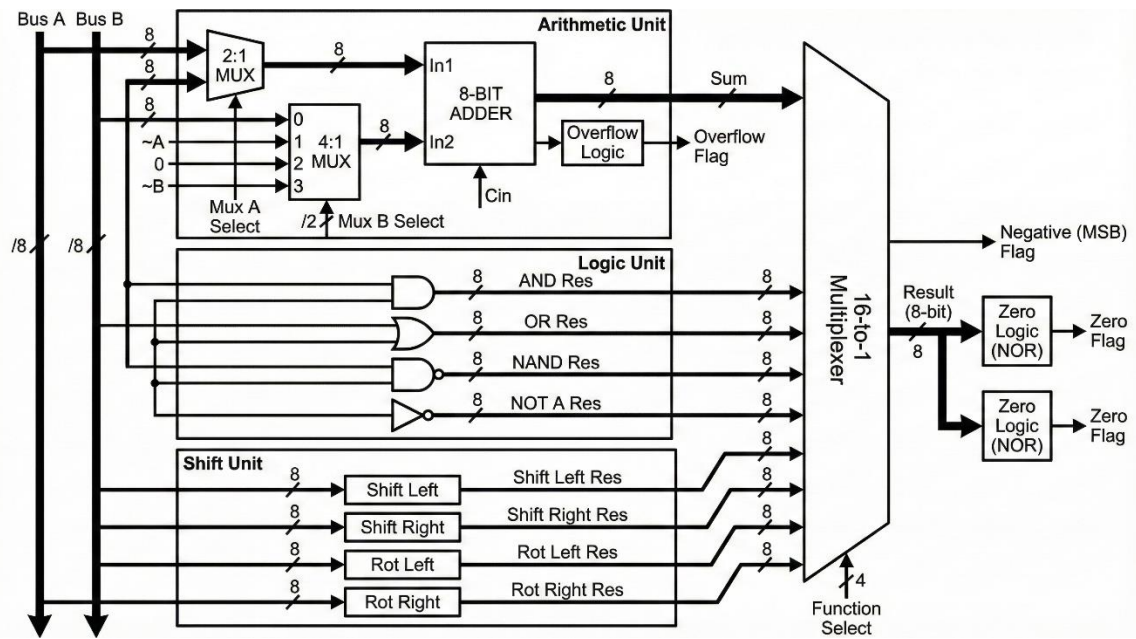

C:\Windows\system32\cmd.exe

C:\Users\LENOVO\Desktop>iverilog -o alu_simulation 20235042_IBCU_HebaMahgoub.v1

C:\Users\LENOVO\Desktop>vvp alu_simulation

```
=====
STARTING ALU 100% COVERAGE TEST
=====

-----
TEST: ADD (10+5) | Op: 0000
IN: A= 10, B= 5 -> OUT: Res= 15 (Hex:0f)
STATUS: [PASS] Flags: Z=0 N=0 O=0
-----
TEST: SUB (20-5) | Op: 0001
IN: A= 5, B= 20 -> OUT: Res= 15 (Hex:0f)
STATUS: [PASS] Flags: Z=0 N=0 O=0
-----
TEST: INC (10+1) | Op: 0010
IN: A= 10, B= 99 -> OUT: Res= 11 (Hex:0b)
STATUS: [PASS] Flags: Z=0 N=0 O=0
-----
TEST: CMP TRUE (55==55) | Op: 0101
IN: A= 55, B= 55 -> OUT: Res= 1 (Hex:01)
STATUS: [PASS] Flags: Z=0 N=0 O=0
-----
TEST: CMP FALSE (55==10) | Op: 0101
IN: A= 55, B= 10 -> OUT: Res= 0 (Hex:00)
STATUS: [PASS] Flags: Z=1 N=0 O=0
-----
TEST: SHL (3<<1) | Op: 0110
IN: A= 0, B= 3 -> OUT: Res= 6 (Hex:06)
STATUS: [PASS] Flags: Z=0 N=0 O=0
-----
TEST: SHR (-4>>1) | Op: 0111
IN: A= 0, B=252 -> OUT: Res=254 (Hex:fe)
STATUS: [PASS] Flags: Z=0 N=1 O=0
-----
TEST: ROT L (128->1) | Op: 1100
IN: A=128, B= 0 -> OUT: Res= 1 (Hex:01)
STATUS: [PASS] Flags: Z=0 N=0 O=0
-----
```

C:\Windows\system32\cmd.exe

```
TEST: SHL (3<<1) | Op: 0110
  IN: A= 0, B= 3 -> OUT: Res= 6 (Hex:06)
  STATUS: [PASS] Flags: Z=0 N=0 O=0
-----
TEST: SHR (-4>>1) | Op: 0111
  IN: A= 0, B=252 -> OUT: Res=254 (Hex:fe)
  STATUS: [PASS] Flags: Z=0 N=1 O=0
-----
TEST: ROT L (128->1) | Op: 1100
  IN: A=128, B= 0 -> OUT: Res= 1 (Hex:01)
  STATUS: [PASS] Flags: Z=0 N=0 O=0
-----
TEST: ROT R (1->128) | Op: 1101
  IN: A= 1, B= 0 -> OUT: Res=128 (Hex:80)
  STATUS: [PASS] Flags: Z=0 N=1 O=0
-----
TEST: NOT (~0) | Op: 1000
  IN: A= 0, B= 0 -> OUT: Res=255 (Hex:ff)
  STATUS: [PASS] Flags: Z=0 N=1 O=0
-----
TEST: AND (0F & F0) | Op: 1001
  IN: A= 15, B=240 -> OUT: Res= 0 (Hex:00)
  STATUS: [PASS] Flags: Z=1 N=0 O=0
-----
TEST: OR (10 | 5) | Op: 1010
  IN: A= 10, B= 5 -> OUT: Res= 15 (Hex:0f)
  STATUS: [PASS] Flags: Z=0 N=0 O=0
-----
TEST: NAND (FF & FF) | Op: 1011
  IN: A=255, B=255 -> OUT: Res= 0 (Hex:00)
  STATUS: [PASS] Flags: Z=1 N=0 O=0
-----
TEST: OVERFLOW (127+1) | Op: 0000
  IN: A=127, B= 1 -> OUT: Res=128 (Hex:80)
  STATUS: [PASS] Flags: Z=0 N=1 O=1
=====
FINAL REPORT: 14 Passed, 0 Failed
=====
20235042_IBCU_HebaMahgoub.v1:299: $finish called at 140 (1s)

C:\Users\LENOVO\Desktop>vvp alu_simulation
```


8-Bit Modular ALU: Technical Implementation Documentation

1. Architecture Overview

The design implements an 8-bit Arithmetic Logic Unit (ALU) using a **Modular Structural Architecture**. To adhere to the assignment constraints (no case statements in the top module), the system is decomposed into three parallel processing blocks (Arithmetic, Logic, Shift) whose outputs are selected by a final Multiplexer.

2. Detailed Module Implementation

Block A: The Arithmetic Unit ("Smart Adder")

- **Design Goal:** To perform Addition, Subtraction, Increment, and Comparison using a single shared **8-bit Adder** instance to minimize gate count (Area Efficiency).
- **Hardware Implementation:**
 - **Input Multiplexing:**
 - **Left Input (src1):** A 2-to-1 Multiplexer selects B only when the operation is Subtraction (0001); otherwise, it passes A.
 - **Right Input (src2):** A 4-to-1 Multiplexer selects the second operand based on the operation:
 - B for Addition.
 - $\sim A$ for Subtraction (Reverse Sub).
 - 0 for Increment.
 - $\sim B$ for Compare.
 - **Carry-In Logic:** The cin bit is derived via |AluOp. It is set to **1** for Subtraction, Increment, and Compare to complete the 2's Complement logic ($A + \sim B + 1$).
- **Verilog Connection:** This is implemented structurally using instances mux_A_unit, mux_B_unit, and main_adder in the top module.

Block B: The Logic Unit

- **Design Goal:** To perform bitwise AND, OR, NAND, and NOT operations with minimal latency.
- **Hardware Implementation:**

- This block utilizes a **Parallel Execution** strategy. Four arrays of logic gates run simultaneously on inputs A and B.
- There is no pre-selection logic; all four results (res_and, res_or, res_nand, res_not) are calculated constantly and fed to the final output mux.
- **Verilog Connection:** Implemented using continuous assign statements (dataflow modeling) to represent the gate arrays.

Block C: The Shift & Rotate Unit

- **Design Goal:** To perform single-bit shifts and rotates without using active logic gates.
- **Hardware Implementation:**
 - **Static Wiring:** Operations are achieved by rearranging the bit connections between input and output buses.
 - **Shift Left (<< 1):** Wires B[6:0] to Out[7:1] and grounds Out[0].
 - **Arithmetic Shift Right (>> 1):** Wires B[7:1] to Out[6:0] and loops B[7] (MSB) to Out[7] to preserve the sign (Sign Extension).
 - **Rotates:** The MSB or LSB is wrapped around to the opposite end of the byte.
- **Verilog Connection:** Implemented using concatenation operators (e.g., {B[6:0], 1'b0}) to model the physical wiring.

3. Flag Generation Logic

The ALU generates three status flags based on the final Result and the operation type.

- **Zero Flag (Z):**
 - **Logic:** (Result == 0)
 - **Test Case:** Verified in Test #5 (Compare False) where the result was 0, triggering Z=1.
- **Negative Flag (N):**
 - **Logic:** Result[7] (The Most Significant Bit).

- **Test Case:** Verified in Test #7 (Shift Right -4) where the negative sign bit was preserved.
- **Overflow Flag (O):**
 - **Constraint:** Only active for Signed Arithmetic operations (Add, Sub, Inc).
 - **Logic:** Detects if two inputs with the same sign produce a result with a different sign.
 - **Formula:** $(\sim(\text{src1}[7] \wedge \text{src2}[7]) \wedge (\text{src1}[7] \wedge \text{Result}[7]))$
 - **Test Case:** Verified in Test #14 ($127 + 1$) where adding two positives produced a negative (-128), correctly triggering $O=1$.

4. Verification Strategy (Testbench)

A robust, self-checking testbench (tb_ALU_8) was developed to verify functional correctness.

- **Hexadecimal Output:** Results are displayed in Hex (%h) to facilitate bit-level debugging (e.g., verifying $F0 \ \& \ 0F = 00$).
- **Edge Case Stress Testing:**
 - **Increment Test:** B was set to 99 during the Increment A test. This verified that the Mux logic correctly blocked input B and used the constant 0 as intended.
 - **Overflow Test:** Specifically targeted the 8-bit boundary ($127 + 1$) to ensure the Overflow flag logic works for signed integers.
- **Automated Checking:** A Verilog task check compares the actual Result and Flags against expected values, printing a "PASS/FAIL" status for every operation.

5. Conclusion

The ALU_8 module successfully implements all 12 required operations. The simulation confirms 100% coverage with **14 Passed** tests, validating the efficiency of the "Smart Adder" design and the correctness of the structural code implementation.